

Homework 19 for September 30 2008

Due 8AM on September 30 2008

Physics 221 with Professor Jeff Terry

1. When a potential difference of 150V is applied to the plates of a parallel-plate capacitor, the plates carry a surface charge density of 30 nC/m<sup>2</sup>. What is the spacing between the plates?

$$Q = \frac{\epsilon_0 A}{d} (\Delta V) \quad \frac{Q}{A} = \sigma = \frac{\epsilon_0 (\Delta V)}{d}$$
$$d = \frac{\epsilon_0 (\Delta V)}{\sigma} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(150 \text{ V})}{(30.0 \times 10^{-9} \text{ C}/\text{cm}^2)(1.00 \times 10^4 \text{ cm}^2/\text{m}^2)} = \boxed{4.42 \text{ } \mu\text{m}}$$

2. Two capacitors of 5.0 microfarads and 8.0 microfarads are connected in series to a 24-V battery. What is the potential difference across each capacitor? What if they were connected in parallel?

Any two elements connected in parallel will have the same potential difference – in this case 24V. For series capacitors, it is a little more complex...

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \therefore C = \frac{C_1 C_2}{C_2 + C_1}$$
$$Q_1 = Q_2 = CV = \frac{C_1 C_2 V}{C_2 + C_1}$$
$$V_n = \frac{Q_n}{C_n} = \frac{C_1 C_2 V}{C_n (C_2 + C_1)}$$
$$V_1 = \frac{C_2 V}{(C_2 + C_1)} = \frac{(8.0 \mu\text{F}) 24\text{V}}{13.0 \mu\text{F}} = 15\text{V}$$
$$V_2 = \frac{C_1 V}{(C_2 + C_1)} = \frac{(5.0 \mu\text{F}) 24\text{V}}{13.0 \mu\text{F}} = 9.2\text{V}$$